

b) leírás  $z_2$ -vel

$$z_2 = \frac{u_2}{I} = \frac{u(x=0)}{I(x=0)} = \frac{u_2^+ (1+r_2)}{\frac{u_2^+}{z_0} (1-r_2)} = z_0 \frac{1+r_2}{1-r_2} \quad (\Rightarrow) \quad \boxed{r_2 = \frac{z_2 - z_0}{z_2 + z_0}}$$

- ha  $\text{Re}\{z_2\} \geq 0$ , akkor  $|r_2| \leq 1$

(első rész a  $\delta/\beta$  és  $\delta/\epsilon$  arányból)


3) Speciális leírások

A. Mentes leírás  $z_2 = z_0$  esetén  $r_2 = 0$  (azaz nincs reflexió)  
 $u(x) = u_2^+ e^{\delta x}$  ~~u(x) = u\_2^+ e^{\delta x}~~  $u(z) = u_2^+ e^{\beta z}$

amplitúdó becslés:  $|u(x)| = ?$

most:  $|u(x)| = |u_2^+ \cdot e^{\delta x} \cdot \underbrace{e^{j\beta x}}_{|1|=1}| = |u_2^+| \cdot e^{\delta x}$

$x=0$  után

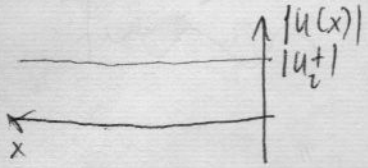

B) Nyitott végű ideális TV (szünetessel leírni)

$$z_2 = \infty \rightarrow r_2 = \lim_{z_2 \rightarrow \infty} \frac{z_2 - z_0}{z_2 + z_0} = 1 \rightarrow$$

teljes reflexió / teljes visszaverődés  
 $|r_2| = 1$

$$u_2^- = u_2^+$$

$$u(x) = u_2^+ (e^{j\beta x} + e^{-j\beta x}) = 2 \cdot u_2^+ \cos(\beta x)$$

ha  $u_2^+ \in \mathbb{R}$  akkor  $u(x, t) = \text{Re}\{2 \cdot u_2^+ \cos \beta x \cdot e^{j\omega t}\} = 2 \cdot u_2^+ \cdot \cos(\beta x) \cdot \cos(\omega t)$

állóhullám alakul ki  $\rightarrow$  költési helyek v. csomópontok

$$u(x, t) = 0 \quad \forall t \Leftrightarrow \cos(\beta x) = 0 \Rightarrow \beta x = \frac{\pi}{2} + k\pi = \frac{\pi}{2} (2k+1) \Rightarrow x = \frac{\pi}{2\beta} (2k+1) = \frac{\lambda}{4} (2k+1)$$

$\lambda = \frac{2\pi}{\beta}$

Mi történik a drámmal

$$I(x) = \frac{U_2^+}{Z_0} (e^{j\beta x} - e^{-j\beta x}) = 2j \frac{U_2^+}{Z_0} \sin \beta x$$

$$i(x,t) = \text{Re} \left\{ 2 \cdot e^{j\omega t} \cdot \frac{U_2^+}{Z_0} \sin \beta x \cdot e^{j\omega t} \right\} = -\frac{2U_2^+}{Z_0} \sin(\beta x) \sin(\omega t)$$

egek zems helyei  $i(x,t) = 0 \quad \forall t \rightarrow \sin \beta x = 0$

$$\beta x = k\pi$$

$$x = \frac{k\pi}{\beta} = k \cdot \frac{\lambda}{2}$$

Mi van amikor  $x = \frac{\lambda}{4} (2k+1)$ ?




$$x = \frac{\pi}{2\beta} (2k+1) \rightarrow i = -\frac{2U_2^+}{Z_0} \sin(\omega t) \cdot \sin\left(\frac{\pi}{2\beta} (2k+1) \cdot \beta\right)$$

(u-vel ~~max~~   
 van

$\frac{\pi}{2} \cdot (2k+1) \Rightarrow$  sin-vel extrémum van

ahol u-vel ~~max~~   
 van

ott i-vel maximum van

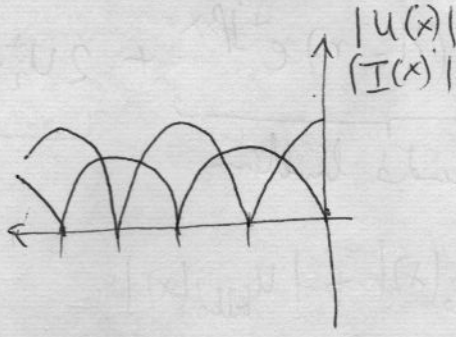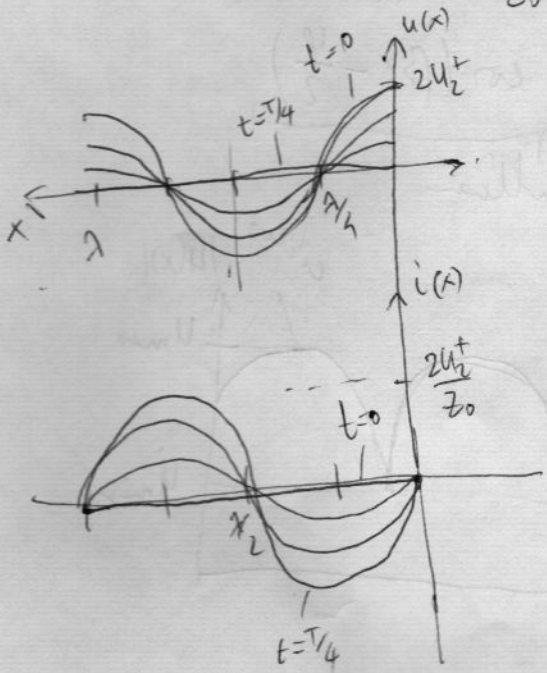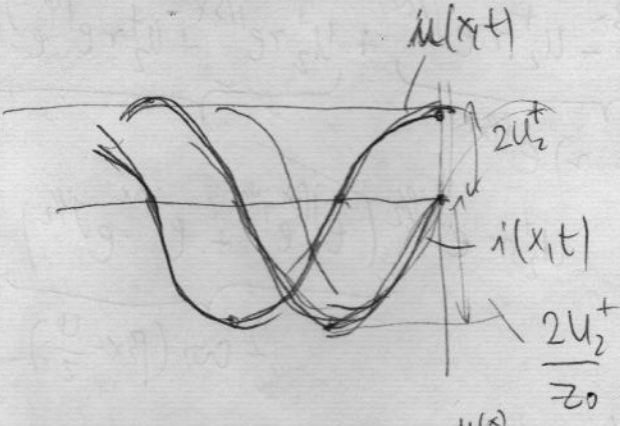

c) Könische zórt (ideális TV)


/11

$$\boxed{Z_2 = 0} \rightarrow \tau_2 = \frac{Z_2 - Z_0}{Z_2 + Z_0} = -1$$

általános alakulási

$$\rightarrow U(x) = U_2^+ (e^{j\beta x} + (-1)e^{-j\beta x}) = 2j \cdot U_2^+ \cdot \sin \beta x$$
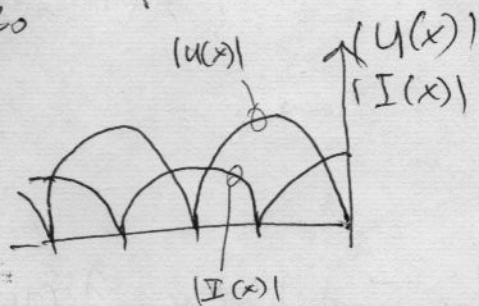
$$\rightarrow I(x) = \frac{U_2^+}{Z_0} (e^{j\beta x} - (-1)e^{-j\beta x}) = 2 \frac{U_2^+}{Z_0} \cos \beta x$$



d) Általános (impedancia) leírás


$$\bar{\tau}_2 = \frac{\bar{Z}_2 - \bar{Z}_0}{\bar{Z}_2 + \bar{Z}_0} = r_2 \cdot e^{j\varphi}, \text{ ahol } r_2 \in \mathbb{R}, \varphi \in [0, 2\pi]$$

$$U(x) = U_2^+ (e^{j\beta x} + r_2 e^{j\varphi} e^{-j\beta x}) = \underbrace{U_2^+ e^{j\beta x} - U_2^+ r_2 e^{j\beta x}}_{U_2^+ (1-r_2) e^{j\beta x}} + \underbrace{U_2^+ r_2 e^{j\beta x} + U_2^+ r_2 e^{j\varphi} e^{-j\beta x}}_{U_2^+ r_2 e^{j\varphi/2} (e^{j\beta x} e^{j\varphi/2} + e^{-j\beta x} e^{j\varphi/2})}$$

$$= U_2^+ (1-r_2) e^{j\beta x} + 2 U_2^+ r_2 e^{j\varphi/2} \cos(\beta x - \frac{\varphi}{2})$$

$$U(x) = \underbrace{U_2^+ (1-r_2) e^{j\beta x}}_{\text{holváltó hullám}} + \underbrace{2 U_2^+ r_2 e^{j\varphi/2} \cos(\beta x - \frac{\varphi}{2})}_{\text{általános}}$$

$$|U(x)| = \underbrace{|U_{\text{holváltó}}(x)|}_{U_2^+ (1-r_2)} + \underbrace{|U_{\text{általános}}(x)|}_{2 U_2^+ r_2 |\cos(\beta x - \frac{\varphi}{2})|}$$

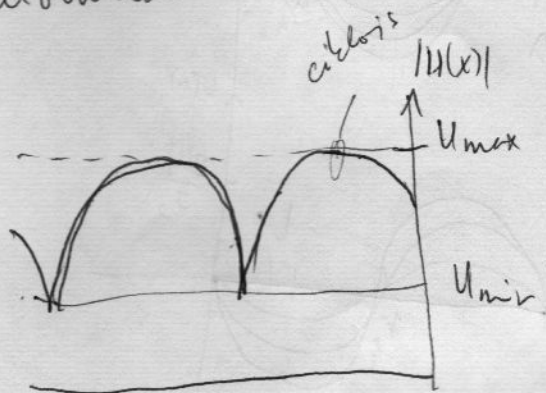

# 5.) Allóhullámok

al def.

$$\boxed{\Gamma = \frac{U_{max}}{U_{min}}}$$

VSWR - Voltage Standing Wave Ratio

$$\Gamma \in [1; \infty]$$

$\Gamma = 1$ , ha  $U_{max} = U_{min} \Rightarrow$  tiszta hulló


$\Gamma \rightarrow \infty$ , ha  $U_{min} \rightarrow 0 \Rightarrow$  tiszta Allóhullám

b) hogyan függ a kocsistól ( $r_2$ -n kocsistól)

$$\Gamma_2 = \Gamma \cdot e^{j\psi}$$

$$u(x) = u_2^+ \cdot (e^{j\beta x} + \Gamma e^{j\psi} e^{-j\beta x}) = u_2^+ \cdot e^{j\beta x} (1 + \Gamma \cdot e^{-j(2\beta x - \psi)})$$

$$|u(x)| = |u_2^+| \cdot |1 + \Gamma e^{-j(2\beta x - \psi)}|$$

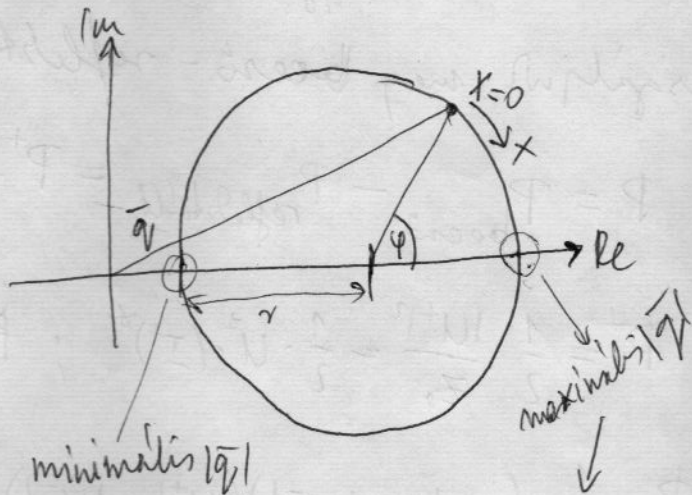

def. alapján

$$\Gamma = \frac{U_{max}}{U_{min}} = \frac{|u_2^+| \cdot |1+r|}{|u_2^+| \cdot |1-r|}$$



$$U_{min} = \min_x (|u(x)|) = |u_2^+| |1-r|$$

$$U_{max} = \max_x |u(x)| = |u_2^+| \cdot |1+r|$$

$$\boxed{\Gamma = \frac{1+|r|}{1-|r|}}$$

megjegyzés:

$$U_{max} = |u_2^+| + |u_2^-| \quad (= |u^+| + |u^-|)$$

$$U_{min} = |u_2^+| - |u_2^-|$$

# Teljesítményváltás (vesztés, ideális TV-n)

$$U(z) = U^+ e^{-j\beta z} + U^- e^{j\beta z}$$

$$I(z) = \frac{U^+}{Z_0} e^{-j\beta z} - \frac{U^-}{Z_0} e^{j\beta z}$$

$\Rightarrow P(z)$

$-C + C^*$  miatt történik képletes

$z$ -nél állandósított teljesítmény

$$P(z) = \frac{1}{2} \operatorname{Re} \{ U(z) \cdot I(z)^* \} = \frac{1}{2} \operatorname{Re} \left\{ \frac{|U^+|^2}{Z_0^*} - \frac{|U^+||U^-|}{Z_0^*} e^{-j\beta z} + \frac{|U^-||U^+|}{Z_0^*} e^{j\beta z} - \frac{|U^-|^2}{Z_0^*} \right\} = \frac{1}{2} \frac{|U^+|^2 - |U^-|^2}{Z_0^*}$$

$\uparrow$   
 $= Z_0$  mert ideális!

$P(z)$  a  $z$ -tól független

viszont megbeszélés - reflektált hengerből

$$P = P_{\text{beszélés}} - P_{\text{reflektált}} = P^+ - P^-$$

$$P^+ = \frac{1}{2} \frac{|U^+|^2}{Z_0} = \frac{1}{2} \cdot U^+ \cdot (I^+)^* ; \quad P^- = \frac{1}{2} \frac{|U^-|^2}{Z_0} = \frac{1}{2} U^- \cdot (I^-)^*$$

$$P = \frac{1}{2Z_0} (|U^+|^2 - |U^-|^2) = \frac{1}{2Z_0} U_{\max} \cdot U_{\min} = \frac{1}{2Z_0} \frac{U_{\max}^2}{\rho}$$




$$\operatorname{ch} \gamma x = \frac{e^{\gamma x} + e^{-\gamma x}}{2} \Rightarrow \frac{e^{j\beta x} + e^{-j\beta x}}{2} = \cos(\beta x)$$

$$\operatorname{sh} \gamma x = \frac{e^{\gamma x} - e^{-\gamma x}}{2} \stackrel{\gamma=j\beta}{\downarrow} \frac{e^{j\beta x} - e^{-j\beta x}}{2} = j \sin(\beta x)$$

8/bis 8/c utans ~~nona~~ ~~for~~ ~~ideali~~ ~~TV~~-re ~~innen~~ ~~abstrakte~~

Idealis TV

$\gamma = j\beta$   
 $l, Z_0$

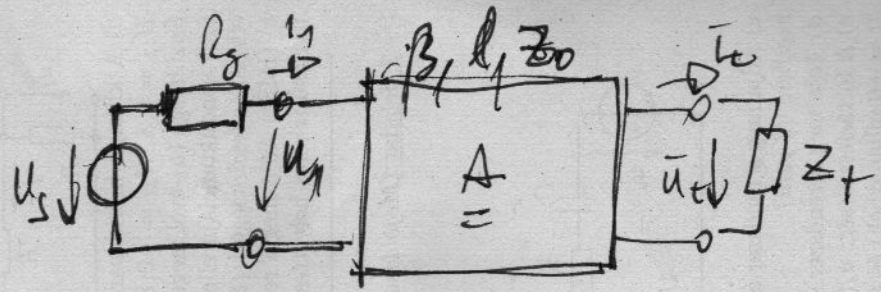

$$A = \begin{pmatrix} \cos \beta l & j Z_0 \sin \beta l \\ j \sin \beta l & \cos \beta l \end{pmatrix}$$

$f = 3 \text{ GHz}$      $\lambda = 0,1 \text{ m}$

$\beta = \frac{\omega}{v} =$

$c = 2,12 \cdot 10^8 \text{ m/s}; f = 3 \text{ GHz}; \omega = 1,885 \cdot 10^{10} \frac{\text{rad}}{\text{s}}$

$\lambda = \frac{c}{f} = 0,0707 \text{ m}$      $\beta = 88,913 \text{ rad/m}$



$Z_0 = 29,27 \Omega; \underline{A} = \begin{pmatrix} 0,8897 & j13,3655 \\ j0,0156 & 0,8897 \end{pmatrix}$   
 ( $\lambda = 0,5$ )

$\bar{u}_s = 10 \text{ V}$   
 $R_g = 0,5 \Omega$   
 $Z_t = 5 \Omega$

$\bar{u}_t = Z_t \cdot \bar{I}_t$   
 $\bar{u}_1 = \bar{u}_s - R_g \cdot I_1$   
 $\bar{u}_1 = A_{11} \bar{u}_2 + A_{12} \bar{I}_2$   
 $\bar{I}_1 = A_{21} \bar{u}_2 + A_{22} \bar{I}_2$

$$\begin{matrix} u_1 & I_1 & u_2 & I_2 \end{matrix} \left\{ \begin{pmatrix} 1 & 0 & -A_{11} & -A_{12} \\ 0 & 1 & -A_{21} & -A_{22} \\ 1 & R_g & 0 & 0 \\ 0 & 0 & 1 & -Z_t \end{pmatrix} \begin{pmatrix} \bar{u}_1 \\ \bar{I}_1 \\ \bar{u}_2 \\ \bar{I}_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ \bar{u}_s \\ 0 \end{pmatrix} \right.$$
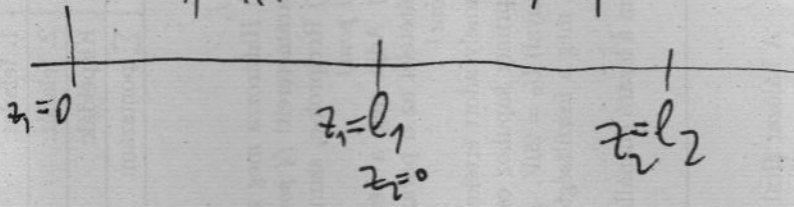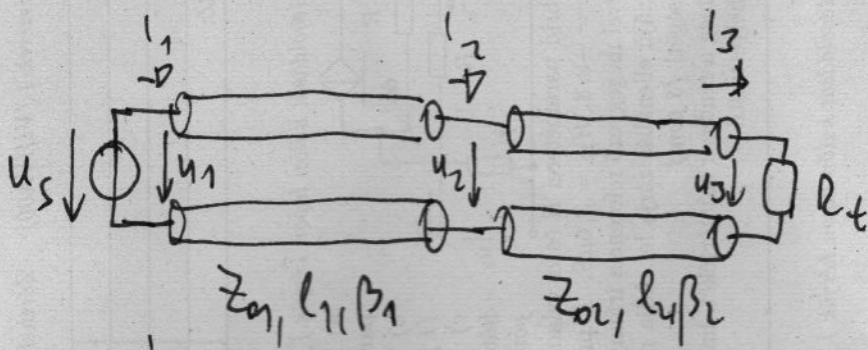
$$f = 800 \text{ MHz} \quad c = 3 \cdot 10^8 \text{ m/s} \quad Z_0 = 50 \Omega \quad \lambda_g = 0,375 \text{ m}$$



a)

$$U_1 = A_{11}^{(1)} U_2 + A_{12}^{(1)} I_2$$

$$I_1 = A_{21}^{(1)} U_2 + A_{22}^{(1)} I_2$$

$$U_2 = A_{11}^{(2)} U_3 + A_{12}^{(2)} I_3$$

$$I_2 = A_{21}^{(2)} U_3 + A_{22}^{(2)} I_3$$

$$U_s = U_1 + I_1 R_g$$

$$U_3 = Z_t \cdot I_3$$

$$\begin{pmatrix} U_1 & I_1 & U_2 & I_2 & U_3 & I_3 \\ 1 & \cdot & -A_{11}^{(1)} & -A_{12}^{(1)} & \cdot & \cdot \\ \cdot & 1 & -A_{21}^{(1)} & -A_{22}^{(1)} & \cdot & \cdot \\ \cdot & \cdot & 1 & \cdot & -A_{11}^{(2)} & -A_{12}^{(2)} \\ \cdot & \cdot & \cdot & 1 & -A_{21}^{(2)} & -A_{22}^{(2)} \\ \cdot & \cdot & \cdot & \cdot & 1 & -Z_t \\ 1 \cdot R_g & 0 & 0 & 0 & 0 & 0 \end{pmatrix} = U_s$$

$$U_1^+ / U_1^- \quad U_2^+ / U_2^-$$

$$U_1(z_1) = U_1^+ e^{-j\beta z_1} + U_1^- e^{j\beta z_1}$$

$$I_1(z_1) = \frac{U_1^+}{Z_{01}} e^{-j\beta z_1} - \frac{U_1^-}{Z_{01}} e^{j\beta z_1}$$

$$U_2(z_2) = U_2^+ e^{-j\beta z_2} + U_2^- e^{j\beta z_2}$$

$$I_2(z_2) = \frac{U_2^+}{Z_{02}} e^{-j\beta z_2} - \frac{U_2^-}{Z_{02}} e^{j\beta z_2}$$

$$U_1 = U_1(0) = U_s - I_1 R_g$$

$$U_1(l_1) = U_2(0)$$


$$I_1(l_1) = I_2(0)$$

$$U_3 = Z_t \cdot I_3$$

$$U_2(l_2) = Z_t \left( \frac{U_2}{I_2}(l_2) \right)$$


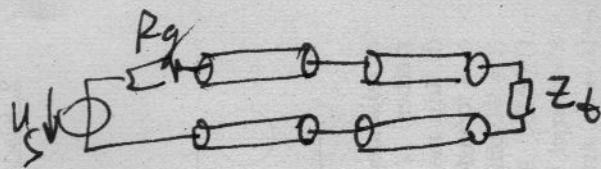
$$① \quad U_1^+ + U_1^- = U_s - R_g \left( \frac{U_1^+}{Z_{01}} - \frac{U_1^-}{Z_{01}} \right)$$




$$② \quad U_1^+ e^{-i\beta_1 l_1} + U_1^- e^{i\beta_1 l_1} = U_2^+ + U_2^-$$

$$③ \quad \frac{U_1^+}{Z_{01}} e^{-i\beta_1 l_1} - \frac{U_1^-}{Z_{01}} e^{i\beta_1 l_1} = \frac{U_2^+}{Z_{02}} - \frac{U_2^-}{Z_{02}}$$

$$④ \quad U_2^+ e^{-i\beta_2 l_2} + U_2^- e^{i\beta_2 l_2} = Z_t \left( \frac{U_2^+}{Z_{02}} e^{-i\beta_2 l_2} - \frac{U_2^-}{Z_{02}} e^{i\beta_2 l_2} \right)$$

$$\begin{pmatrix} U_1^+ & U_1^- & U_2^+ & U_2^- \\ 1 + \frac{R_g}{Z_{01}} & 1 - \frac{R_g}{Z_{01}} & \cdot & \cdot \\ e^{-i\beta_1 l_1} & e^{i\beta_1 l_1} & -1 & -1 \\ \frac{e^{-i\beta_1 l_1}}{Z_{01}} & -\frac{e^{i\beta_1 l_1}}{Z_{01}} & -\frac{1}{Z_{02}} & \frac{1}{Z_{02}} \\ e^{i\beta_2 l_2} & \cdot & e^{-i\beta_2 l_2} \left( 1 - \frac{Z_t}{Z_{02}} \right) & e^{i\beta_2 l_2} \left( 1 + \frac{Z_t}{Z_{02}} \right) \end{pmatrix} \begin{pmatrix} U_1^+ \\ U_1^- \\ U_2^+ \\ U_2^- \end{pmatrix} = \begin{pmatrix} U_s \\ \cdot \\ \cdot \\ \cdot \end{pmatrix}$$
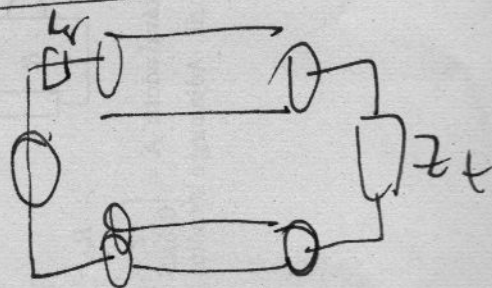
$$U_1^+ + U_1^- = U_s - R_g \left( \frac{U_1^+}{Z_0} - \frac{U_1^-}{Z_0} \right)$$



$$U_1^+ e^{-i\beta l} + U_1^- e^{i\beta l} = Z_t \left( \frac{U_1^+}{Z_0} e^{-i\beta l} - \frac{U_1^-}{Z_0} e^{i\beta l} \right)$$

$$\begin{pmatrix} 1 + \frac{R_g}{Z_0} & 1 - \frac{R_g}{Z_0} \\ e^{-i\beta l} \left( 1 - \frac{Z_t}{Z_0} \right) & e^{i\beta l} \left( 1 + \frac{Z_t}{Z_0} \right) \end{pmatrix} \begin{pmatrix} U_1^+ \\ U_1^- \end{pmatrix} = \begin{pmatrix} U_s \\ 0 \end{pmatrix}$$