

$$-i_1 - i_2 + Cu' = 0$$

$$u_1 - i_1 R_1 - (L_1 i_1' + M \cdot i_2') - u = 0$$

$$-i_2 R_2 + L_2 i_2' + M i_1' + u = 0$$


$$i_1' = \frac{R_2 L_2}{M^2 - L_1 L_2} i_1 + \frac{R_1 M}{M^2 - L_1 L_2} i_2 +$$

$$+ \frac{L_2 - M}{M^2 - L_1 L_2} u - \frac{L_2}{M^2 - L_1 L_2} u_s$$

$$i_2' = -\frac{R_1 M}{M^2 - L_1 L_2} i_1 - \frac{R_2 L_1}{M^2 - L_1 L_2} i_2 +$$

$$+ \frac{L_1 - M}{M^2 - L_1 L_2} u + \frac{M}{M^2 - L_1 L_2} u_s$$
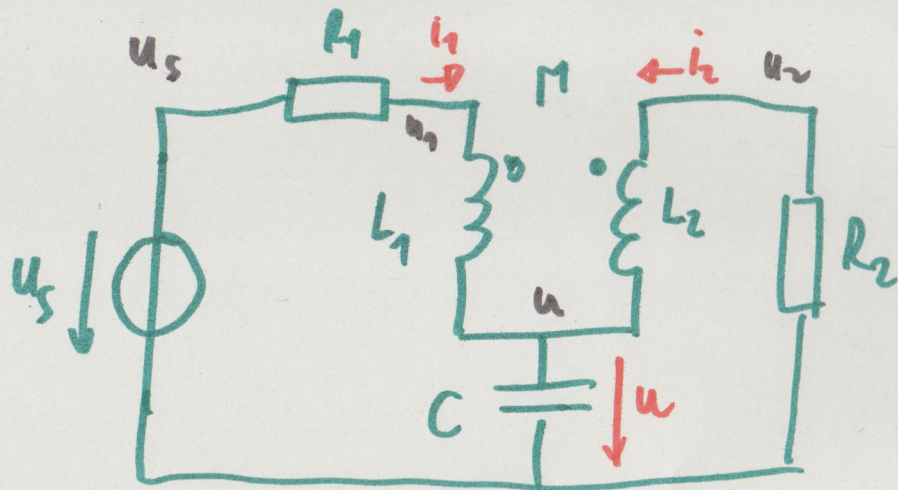
$$u' = \frac{1}{C} i_1 + \frac{1}{C} i_2$$



$$Cu' - i_1 - i_2 = 0$$

$$u_1 = u + L_1 i_1' + M \cdot i_2'$$


$$u_2 = u + L_2 i_2' + M \cdot i_1'$$

$$\frac{u_s}{R_1} + i_1 = 0$$

$$\frac{u_2}{R_2} + i_2 = 0$$

non-ideal
 series circuit
 $L_1 L_2 > M^2$
 $(L_1 L_2 - M^2 > 0)$

$$p = \sqrt{\frac{L_2}{L_1}}$$

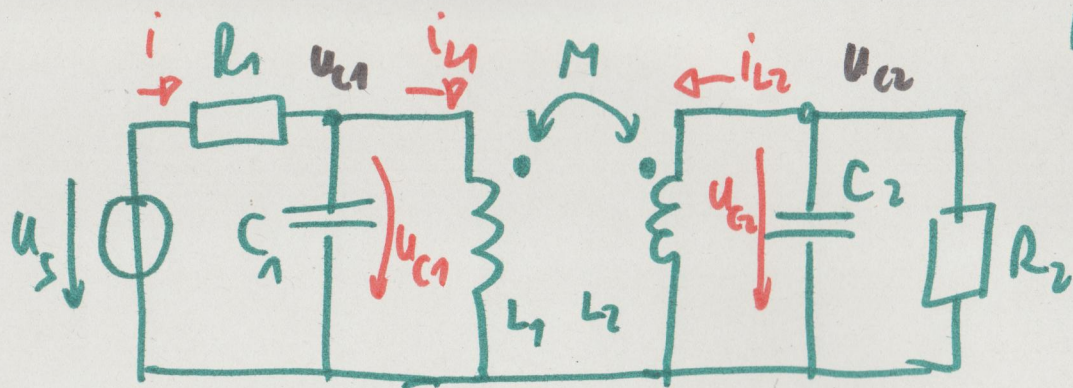

$k, R_1, R_2, L_1, L_2, C_1, C_2, M$
 $R_1 = 2$
 $R_2 = 4$
 $C_1 = 4$
 $C_2 = 2$
 $L_1 = 4$
 $L_2 = 8$
 $M = 1$

$$u_{C1}' = -\frac{1}{L_1 C_1} u_{C1} - \frac{1}{C_1} i_{L1}' + \frac{1}{L_1} u_s$$

$$u_{C2}' = -\frac{1}{L_2 C_2} u_{C2} - \frac{1}{C_2} i_{L2}'$$

~~WWS~~

$$i_{L2}' = \frac{M}{M^2 - L_1 L_2} u_{C1} - \frac{L_1}{M^2 - L_1 L_2} u_{C2}$$

$$i_{L1}' = -\frac{L_2}{M^2 - L_1 L_2} u_{C1} + \frac{M}{M^2 - L_1 L_2} u_{C2}$$

$$C_1 u_{C1}' + i_{L1}' + \frac{u_{C1} - u_s}{R_1} = 0$$

$$C_2 u_{C2}' + i_{L2}' + \frac{u_{C2}}{R_2} = 0$$


$$u_{C1} = L_1 i_{L1}' + M i_{L2}'$$

$$u_{C2} = L_2 i_{L2}' + M i_{L1}'$$

$$\frac{u_{C1}}{M} - \frac{u_{C2}}{L_2} = \left(\frac{L_1}{M} - \frac{M}{L_2} \right) i_{L1}'$$

$$\frac{u_{C1}}{L_1} - \frac{u_{C2}}{M} = \frac{M}{L_1} i_{L2}' - \frac{L_2}{M} i_{L2}'$$
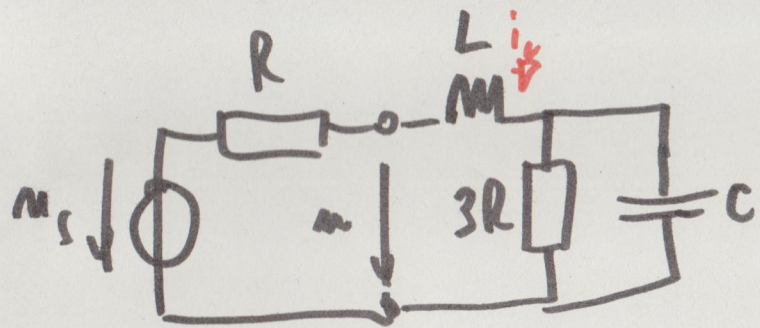
$$i_{L2}' = \frac{M L_1}{M^2 - L_1 L_2} \left(\frac{M u_{C1} - L_1 u_{C2}}{M L_1} \right)$$



$$\textcircled{1} \quad u = u_c + L i_L'$$

$$\textcircled{2} \quad -i_L + \frac{u_c}{3R} + C u_c' = 0$$

$$\textcircled{3} \quad u_s - i_L \cdot R = u$$

$$\left. \begin{array}{l} \textcircled{1} \\ \textcircled{3} \end{array} \right\} \quad u_s - i_L \cdot R = u_c + L i_L' \rightarrow L i_L' = -R i_L - u_c + u_s$$

$$i_L' = -\frac{R}{L} i_L - \frac{1}{L} u_c + \frac{1}{L} u_s$$

$$\textcircled{2} \rightarrow C u_c' = i_L - \frac{1}{3R} u_c \rightarrow$$

$$u_c' = \frac{1}{C} i_L - \frac{1}{3RC} u_c$$


$u_c, i_L, u_a, i_a, u_b, i_b, u_r$

AVL 2.3-7

$$u_c = -\frac{n}{C} i_L + \frac{1}{C} i_s$$

$$i_L = \frac{n}{L} u_c - \frac{R}{L} (n^2 - 2n + 1) i_L + \frac{R}{L} (1 - n) i_s$$

$$u_r = -R(n-1) i_L + R i_s$$

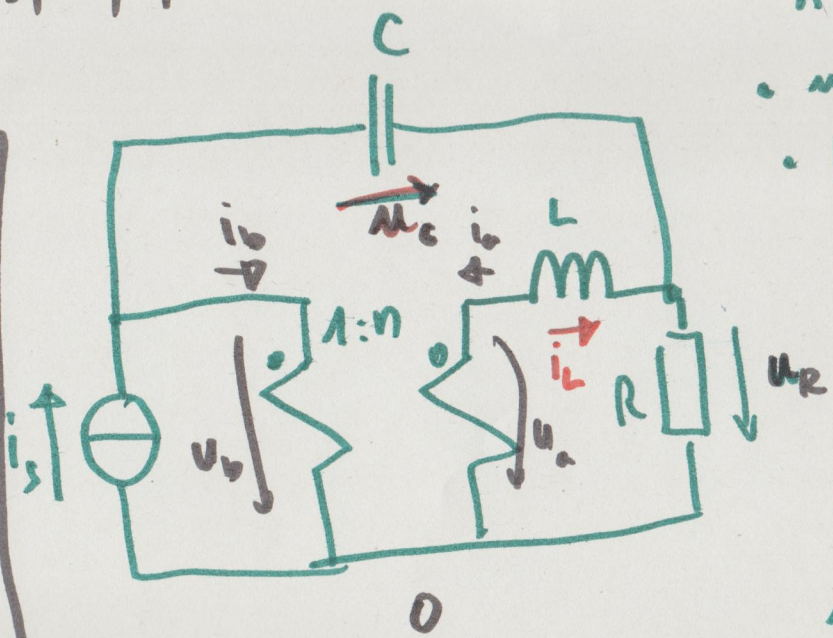

- n_R
- L, C, n adott
- R milyen értékekben =
- transziens
- lezó jellegű

$$\underline{A} = \begin{pmatrix} 0 & -\frac{n}{C} \\ \frac{n}{L} & -\frac{R}{L} (n^2 - 2n + 1) \end{pmatrix}$$

$$\begin{vmatrix} \lambda & n/C \\ n/L & \lambda + \frac{R}{L} (n^2 - 2n + 1) \end{vmatrix} = \lambda \left(\lambda + \frac{R}{L} (n^2 - 2n + 1) \right) + \frac{n^2}{LC}$$

$$\text{lezó ha } \left(\frac{R}{L} (n^2 - 2n + 1) \right)^2 - 4 \cdot \frac{n^2}{LC} < 0$$

$i_a = -i_L$ ← implícite felismerés

$u_a = n \cdot u_b$

$i_b = n \cdot i_L$

$-C u_c' + \frac{u_r}{R} + -i_L = 0$

$-i_s + i_b + C u_c' = 0$


$u_a - L i_L' - u_r = 0$

$u_r + u_c - u_b = 0$

$$\left(\frac{R}{L}\right)^2 (2n^2 - 2n + 1)^2 < \frac{4n^2}{LC}$$

$$R^2 < \frac{4n^2 \cdot L/C}{(n-1)^2} = R_h^2$$


R > 0 feltetés

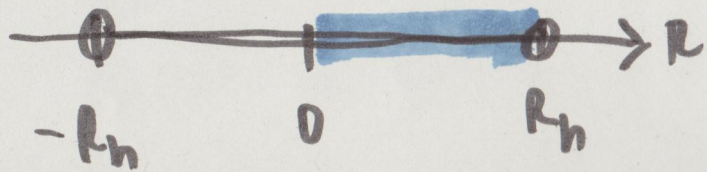

$$\text{ahol } R_h = \sqrt{\frac{L}{C}} \cdot \frac{2n}{n-1}$$

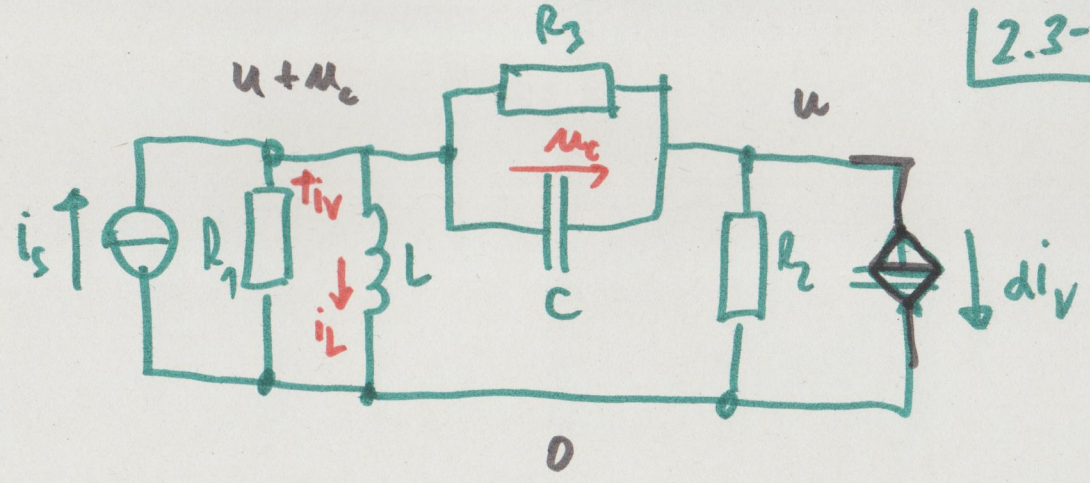2.3+
folyt.

$$\left. \begin{aligned} \textcircled{1} \quad -i_s + \frac{u+u_c}{R_1} + i_L + C u_c' + \frac{u_c}{R_3} &= 0 \\ \textcircled{2} \quad d \cdot \frac{u+u_c}{R_1} + \frac{u}{R_2} - C u_c' - \frac{u_c}{R_3} &= 0 \\ \textcircled{3} \quad u+u_c &= L i_L' \end{aligned} \right\}$$



$$\textcircled{1} + \textcircled{2}: \quad -i_s + (1+d) \frac{u+u_c}{R_1} + i_L + \frac{u}{R_2} = 0$$


$$u \left(\frac{1+d}{R_1} + \frac{1}{R_2} \right) + i_L + \frac{1+d}{R_1} u_c - i_s = 0$$

$$u = \frac{-i_L - \frac{1+d}{R_1} u_c + i_s}{\frac{1+d}{R_1} + \frac{1}{R_2}}$$

$$\frac{-i_L(R_1 R_2) - (1+d)R_2 u_c + R_1 R_2 i_s}{(1+d)R_2 + R_1}$$

$$u_c' = - \frac{R_1 + R_2(1+d) + R_3}{C \cdot R_3 \cdot (R_1 + (1+d)R_2)} u_c - \frac{R_3 \cdot (R_1 + dR_2)}{C \cdot R_1 (R_1 + R_2(1+d))} i_L + \frac{R_1 + dR_2}{C \cdot (R_1 + (1+d)R_2)} i_s$$
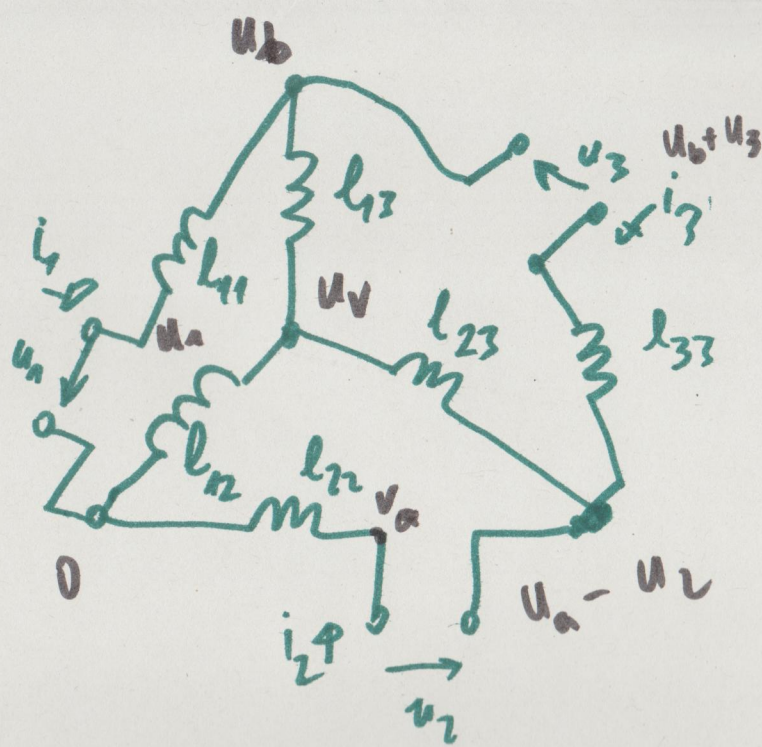
$$i_L' = - \frac{R_1 / (R_1 + (1+d)R_2)}{L} u_c - \frac{R_1 R_2}{L (R_1 + (1+d)R_2)} i_L + \frac{R_1 R_2}{L (R_1 + (1+d)R_2)} i_s$$



Net isoval any
a function of $\boxed{2.3^* = 3}$

$$u_j = \sum_{k=1}^3 L_{jk} \cdot i_k'$$

$k=1, 2, 3$

- indutiv 3-løops
- indutiv 3-løops
- karakteristikk $L_{ij}!$