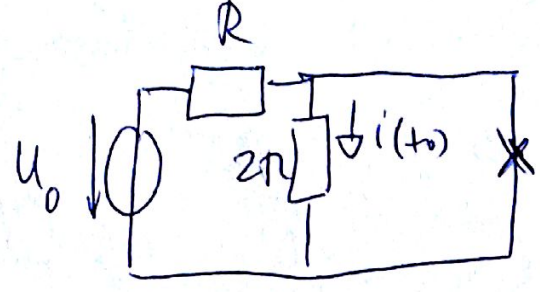


1) a)  $t = +0$




$i'_L(0) = 0 \Rightarrow$  *notwendig*  
 $i'(t_0) = \frac{U_0}{3R} = \frac{10}{15} = \frac{2}{3} \text{ mA}$

$t \rightarrow \infty$



$i'(\infty) = 0$

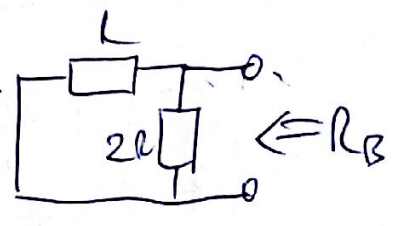

$R_B = R \times 2R = \frac{2R}{3}$   
 $\tau = \frac{L}{R_B} = \frac{3L}{2R} = \frac{3 \cdot 2}{2 \cdot 5} = \frac{3}{5} \text{ ms}$

$i(t) = \varepsilon(t) \left( 0 + \left( \frac{2}{3} - 0 \right) e^{-t/0,6} \right) \text{ mA}$

b.)  $t = -0$  (messigpunkt a) - belii  $\infty$ -vel)


$i'_L = \frac{U_0}{R} \quad i'(-0) = 0$

$t = +0$



$i(t_0) = \frac{R \times 2R}{2R} \cdot \frac{U_0}{R} = \frac{2R/3}{2R} \cdot \frac{U_0}{R} = \frac{U_0}{3R} = \frac{2}{3} \text{ mA}$

$i_\infty = 0$  (wideren form!)

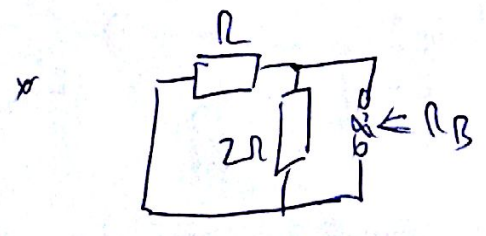


$R_B = R \times 2R = \frac{2R}{3}$   
 $\tau = \frac{L}{R_B} = \frac{3L}{2R} = 0,6 \mu\text{s}$

$i(t) = \begin{cases} 0 & t < 0 \\ \frac{U_0}{3R} e^{-t/\tau} = \frac{2}{3} e^{-t/0,6} & t > 0 \end{cases}$


2/a.)  $t < 0$  energies,  $u_C(0) = 0; U = 0$

$t = +0$

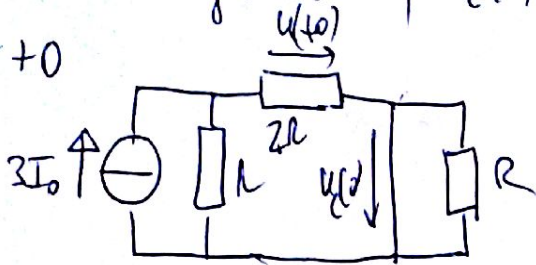


$$u(t=0) = (2R \times R) \cdot 3I_0 = \frac{2R}{3} \cdot 3I_0 = 2RI_0 = 40V$$

$t \rightarrow \infty$

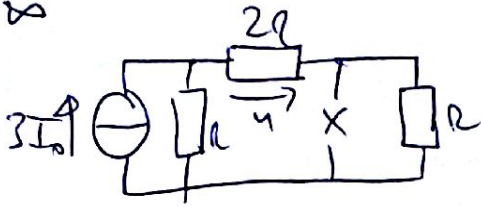

$$u_\infty = 3I_0 \cdot \underbrace{(3R \times R)}_{\frac{3R}{4}} \cdot \underbrace{\frac{2R}{2R+R}}_{\frac{2}{3}} = \frac{I_0 R 3}{2} = 30V$$

$R_B$ :

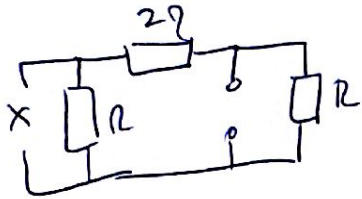

$$R_B = R \times (2R + R) = \frac{3R}{4} = \frac{3}{2} R \Omega$$


$$\tau = C \cdot R_B = \frac{3RC}{4} = \frac{9}{20} \mu s = 0,45 \mu s$$

$$u(t) = (30 + (40 - 30) \cdot e^{-t/0,45}) \epsilon(t)$$


1/b. atterpunkt (  $t < 0$  mesurpunkt an a) - beti d'kond' sult a'kapp'at' )

$$u_C(0) = 3I_0 \cdot \frac{3R}{4} \cdot \frac{1}{3} = \frac{3RI_0}{4}$$

$t = +0$

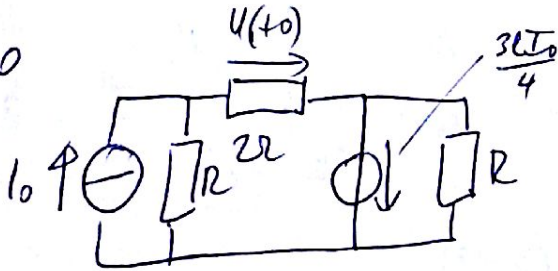

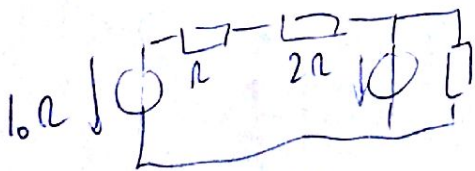
$$u(t=0) = \frac{2}{3} \cdot \left( 10R - \frac{3RI_0}{4} \right) = \frac{4I_0 R}{16} = \frac{20}{6} V \approx 3,33V$$




$$R_B = \frac{3R}{4}; \tau = C \cdot R_B = \dots = 0,45 \mu s$$

$t \rightarrow \infty$

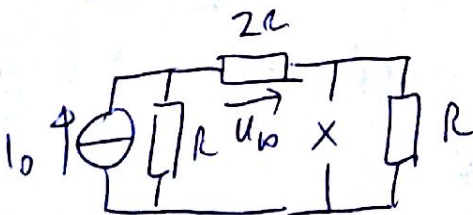

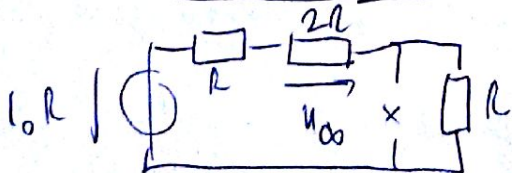
$$u_\infty = \frac{2}{4} \cdot 10R = \frac{10R}{2} = 10V$$



$$u(t) = \begin{cases} 30, & t < 0 \\ 10 + \left( \frac{20}{6} - 10 \right) e^{-t/0,45} & t \geq 0 \end{cases}$$

$-\frac{40}{6} \approx -6,66$

3.)  $\alpha v_L - b v_I$

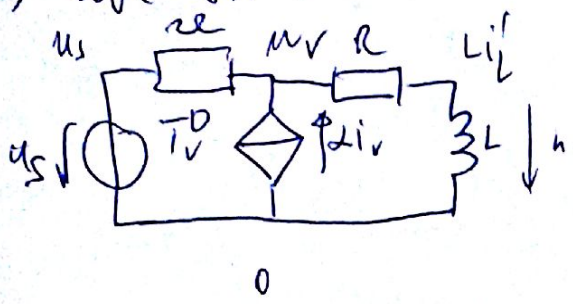

$$\left. \begin{aligned} ① u_v &= L i_L' + R \cdot i_L \\ ② i_L - \alpha i_v - i_v &= 0 \\ ③ u_v &= u_s - 2R \cdot i_v \end{aligned} \right\} ④ u = L i_L'$$

invariant:  $i_v, i_L', u_v, u$  ②  $\rightarrow$   $i_v = \frac{i_L}{1+\alpha}$   $i$   $u_v = \dots$  *neem ártokos számok*

$$L i_L' + R \cdot i_L = u_s - 2R \cdot \frac{i_L}{1+\alpha}$$

$$u = L i_L' = - \underbrace{\left(1 + \frac{2}{1+\alpha}\right)}_{\frac{3+\alpha}{1+\alpha}} R i_L + u_s$$


$$i_L' = - \frac{3+\alpha}{1+\alpha} \frac{R}{L} i_L + \frac{1}{L} u_s$$

$$\lambda = - \frac{3+\alpha}{1+\alpha} < 0 \quad \frac{3+\alpha}{1+\alpha} > 0 \rightarrow \left. \begin{aligned} 3+\alpha > 0 \\ 1+\alpha > 0 \end{aligned} \right\} \left. \begin{aligned} \alpha > -3 \\ \alpha > -1 \end{aligned} \right\} \alpha > -1$$


$$\downarrow \left. \begin{aligned} 3+\alpha < 0 \\ 1+\alpha < 0 \end{aligned} \right\} \left. \begin{aligned} \alpha < -3 \\ \alpha < -1 \end{aligned} \right\} \alpha < -3$$

Stabilitás:  $\alpha < -3$  vagy  $\alpha > -1$

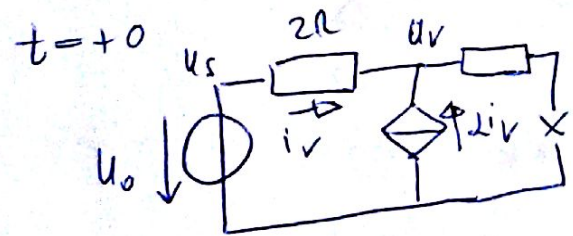válasz függvények alapján  $t < 0$  energiamentes  $\Rightarrow i_L = 0$



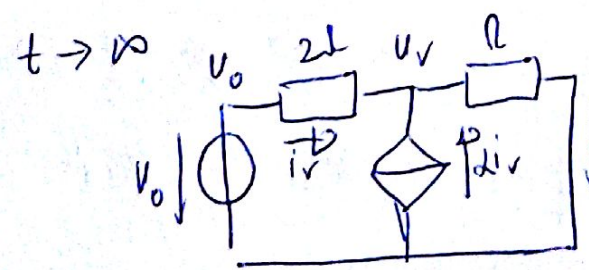
$i_v = 0$  mert  $u = 0$   
 $-i_v - \alpha i_v = 0$   
 $i_L$



$u_v = R \cdot (1+\alpha) i_v$   
 $2R i_v = u_0 - (1+\alpha) R i_v$   
 $(3+\alpha) R i_v = u_0$   
 $i_v = \frac{u_0}{R(3+\alpha)}$


4.)  $i_L(0) = 0$

$t = +0$

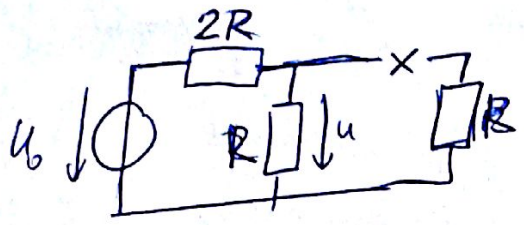


$u(+0) = \frac{1}{3} U_0$

$t \rightarrow \infty$

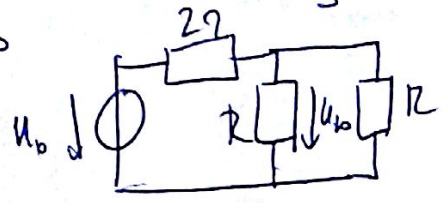

$u_{\infty} = \frac{R/2}{2R + R/2} U_0 = \frac{1}{5} U_0$

$R_B$ :

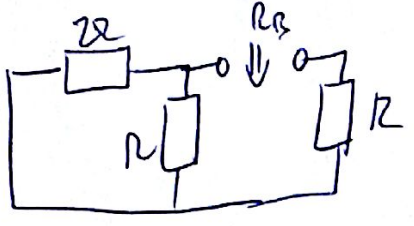


$R_B = (R \times 2R) + R = \frac{2R}{3} + R = \frac{5R}{3}$



$\tau = \frac{L}{R_B} = \frac{0.1 \cdot 3}{0.01 \cdot 5} = \frac{30}{5} = 6 \mu s$

$u(t) = \varepsilon(t) \cdot \left( \frac{U_0}{5} + \left( \frac{U_0}{3} - \frac{U_0}{5} \right) e^{-t/\tau} \right) = \varepsilon(t) \left( \frac{U_0}{5} + \frac{2U_0}{15} e^{-t/\tau} \right)$

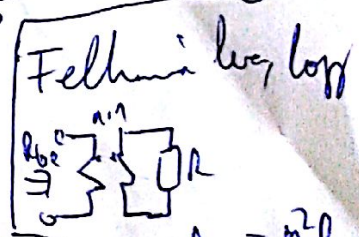$y(t) = \varepsilon(t) \cdot \left( \frac{U_0}{5} + \frac{2U_0}{15} e^{-t/\tau} \right) - \varepsilon(t-\tau) \cdot \left( \frac{U_0}{5} + \frac{2U_0}{15} e^{-(t-\tau)/\tau} \right)$



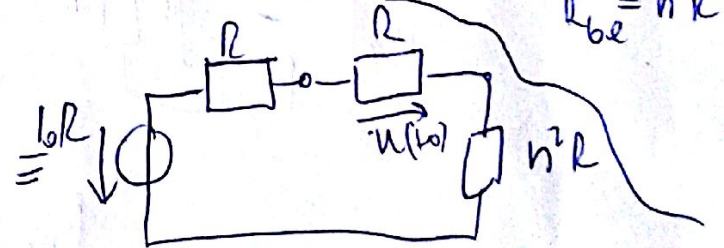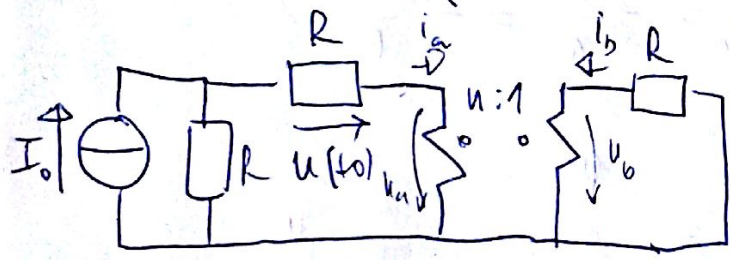5.)  $t = +0 - \tau$  ( $t < 0 - \tau$  energie-neutral  $u_c(0) = 0$ )




$t \rightarrow \infty \rightarrow \frac{1}{\tau} \rightarrow \times$  ann  $i_b = 0 \Rightarrow i_a = 0$

$u(\infty) = 0$

$u(t_0) = \frac{R}{R+R+n^2 R} I_0 R = \frac{1}{n^2+2} I_0 R$

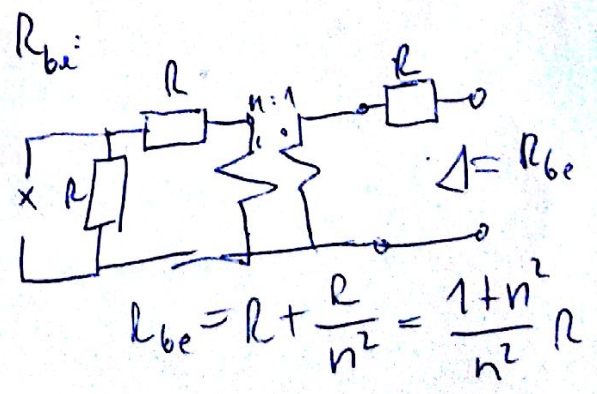$u(t) = \left( 0 + \left( \frac{I_0 R \cdot 1}{2+n^2} \right) e^{-t/\tau} \right) \varepsilon(t)$



$\tau = C \cdot R_{be} = RC \cdot \frac{n^2+1}{n^2}$