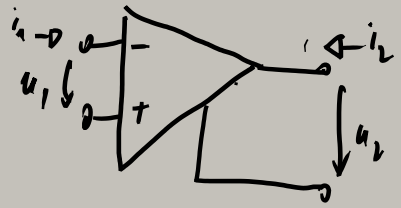



Ideális erősítő

ide nem tudunk egyszerűen felírni



$u_1 = 0 \rightarrow +i_1 -$ áramok potenciálján

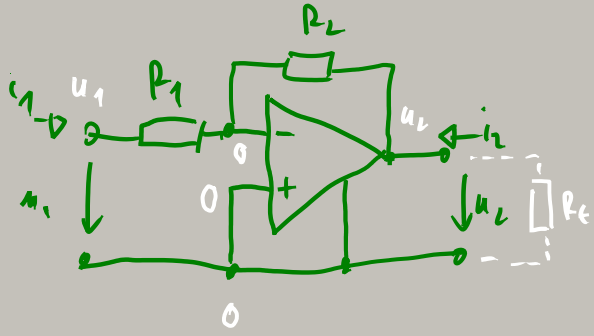
$i_2 = 0 \rightarrow$ minnen befolyó áram



$$\frac{u_2}{u_1} = -\frac{R_2}{R_1}$$

$$u_2 = -\frac{R_2}{R_1} \cdot u_1$$
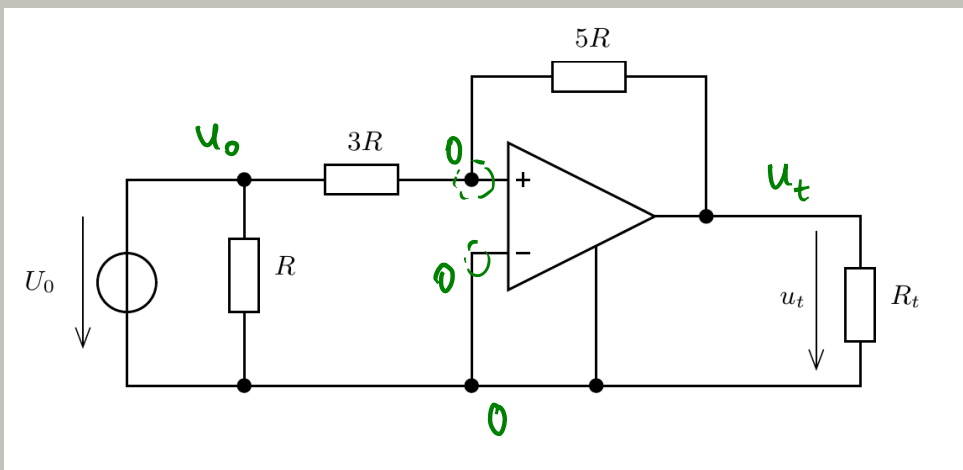
$$\frac{0 - u_1}{R_1} + \frac{0 - u_2}{R_2} = 0$$




$$U_0 = 10V; R = 2k\Omega; R_t = 4k\Omega$$

$$\frac{0 - u_0}{3R} + \frac{0 - u_t}{5R} = 0$$

$$u_t = -\frac{5R}{3R} \cdot u_0 = -\frac{5}{3} u_0$$

$$u_t = -16,66V$$

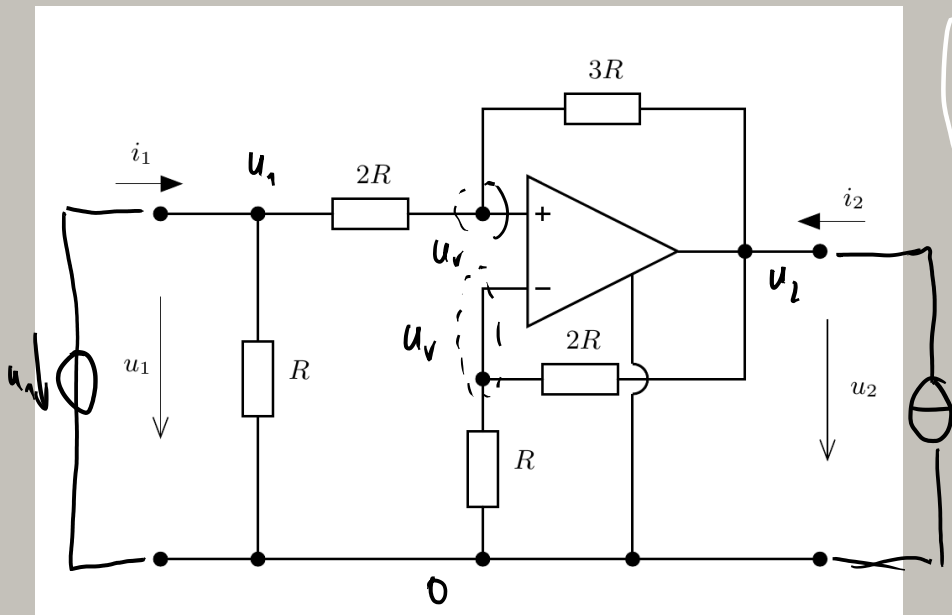

$$\begin{pmatrix} i_1 \\ u_2 \end{pmatrix} = K \cdot \begin{pmatrix} u_1 \\ i_2 \end{pmatrix}$$

$$\textcircled{1} \frac{u_v}{R} + \frac{u_v - u_2}{2R} = 0 \rightarrow u_v = \frac{u_2}{3}$$

$$\textcircled{2} -i_1 + \frac{u_1}{2} + \frac{u_1 - u_v}{2R} = 0$$

$$\textcircled{3} \frac{u_v - u_1}{2R} - \frac{u_v - u_2}{3R} = 0$$

→ megoldásul $\textcircled{1}$ és $\textcircled{3}$

$$u_2 = -9u_1$$

$$i_1 = \frac{3}{R}u_1$$


$$K = \begin{pmatrix} 3/R & 0 \\ -9 & 0 \end{pmatrix}$$

$$i = G \cdot u = \frac{1}{R} \cdot u$$

$$\textcircled{1} -i_1 + G_1 \cdot (u_1 - u_v) = 0$$

$$\textcircled{2} G_3(0 - u_v) + G_5(0 - u_2) = 0$$
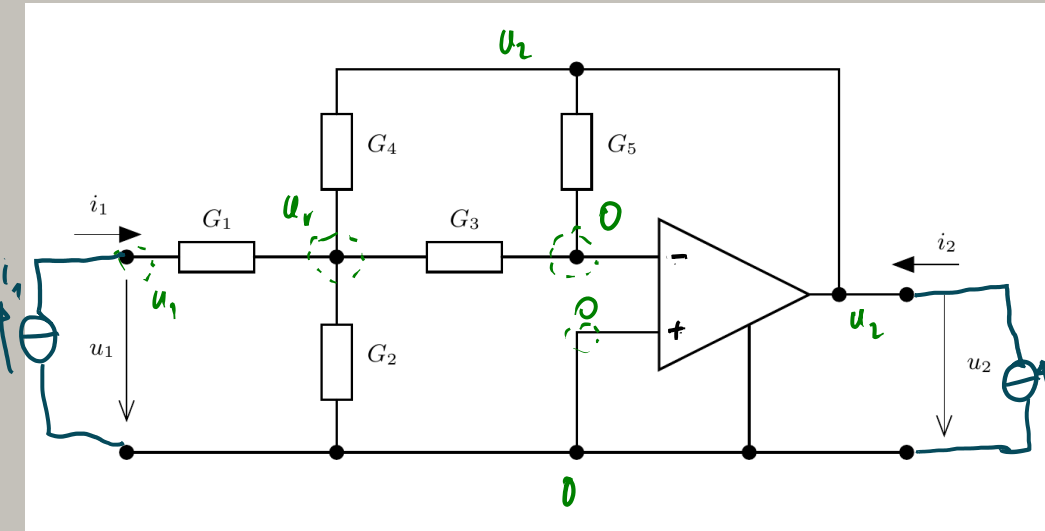
$$\textcircled{3} G_1(u_v - u_1) + G_2 \cdot u_v + G_3(u_v) + G_4 \cdot (u_v - u_2) = 0$$




$$\textcircled{3} \rightarrow u_v = \frac{G_1}{G_1 + G_2 + G_3 + G_4} \cdot u_1 + \frac{G_4}{G_1 + G_2 + G_3 + G_4} \cdot u_2$$

$$\textcircled{2} u_2 = \frac{-G_3}{G_4 + \frac{G_5}{G_3} \cdot (G_1 + G_2 + G_3 + G_4)} \cdot u_1$$


$$\textcircled{1} \rightarrow i_1 = \frac{1}{R} \cdot u_1$$

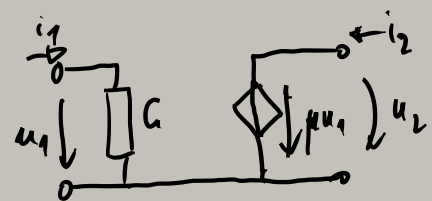- I $i_1 = G \cdot u_1$
 - II $u_2 = \mu \cdot u_1$
- } innen linear
} gewichtet




weitergeleitet
weitergeformt
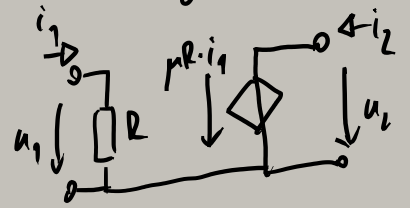
$$\left. \begin{aligned} u_1 &= \frac{1}{G} \cdot i_1 = R \cdot i_1 \\ u_2 &= \mu \cdot R \cdot i_1 \end{aligned} \right\}$$



ausgewertet
weitergeformt

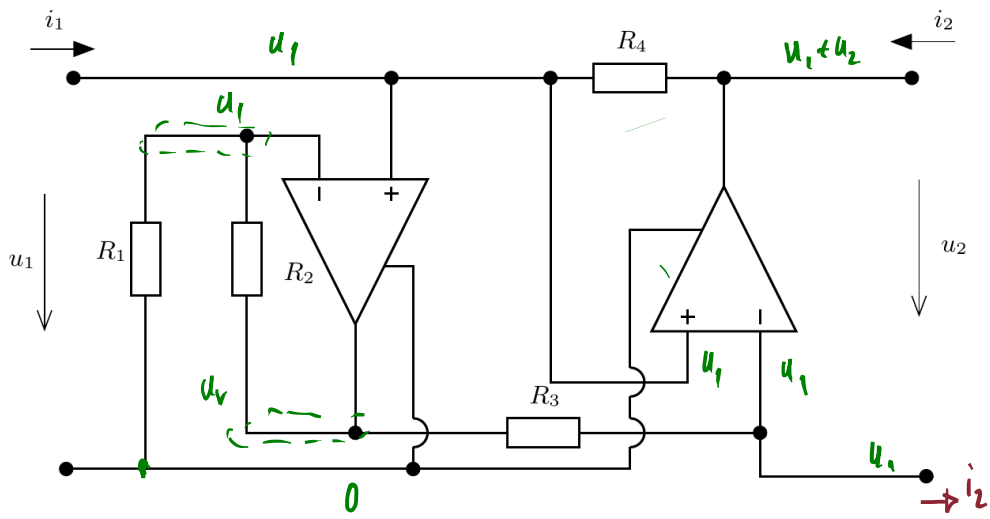

$R \rightarrow$

$$\textcircled{1} -i_1 + \frac{u_1 - (u_1 + u_2)}{R_4} = 0$$

$$\textcircled{2} i_2 + \frac{u_1 - u_V}{R_3} = 0$$

$$\textcircled{3} \frac{u_1}{R_1} + \frac{u_1 - u_V}{R_2} = 0$$

$$\textcircled{3} \Rightarrow u_V = \left(1 + \frac{R_2}{R_1}\right) u_1$$

$$\textcircled{1} -i_1 + \frac{-u_2}{R_4} = 0 \Rightarrow u_2 = -R_4 i_1$$

$$\textcircled{2} i_2 + \frac{1}{R_3} \left(u_1 - \frac{R_1 + R_2}{R_1} \cdot u_1 \right) = 0 \Rightarrow u_1 = \frac{R_1 R_3}{R_2} \cdot i_2$$

$$u_1 = \frac{R_1 R_3}{R_2} \cdot i_2$$

$$u_2 = -R_4 \cdot i_1$$

generator $\left. \begin{matrix} u_1 = -r \cdot i_2 \\ u_2 = r \cdot i_1 \end{matrix} \right\}$

$$\rightarrow \text{für } \frac{-R_1 R_3}{R_2} = -R_4 \Rightarrow R_1 R_3 = R_2 R_4$$

teilerähnliche Struktur

generator, aber

$$r = -R_4 \quad \text{oder} \quad r = -\frac{R_1 R_3}{R_2}$$