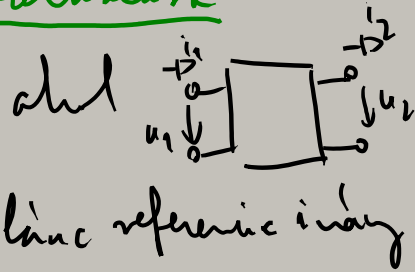


Lineare Transformationen


$$1) \underline{A} \rightarrow \begin{pmatrix} u_1 \\ i_1 \end{pmatrix} = \underline{A} \cdot \begin{pmatrix} u_2 \\ i_2 \end{pmatrix}$$



lineare Referenzierung


$$\begin{pmatrix} u_2 \\ i_2 \end{pmatrix} = \underline{B} \cdot \begin{pmatrix} u_1 \\ i_1 \end{pmatrix} \Leftrightarrow \underline{B}^{-1} \cdot \begin{pmatrix} u_2 \\ i_2 \end{pmatrix} = \underline{E} \cdot \begin{pmatrix} u_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} u_1 \\ i_1 \end{pmatrix}$$

$\underline{B}^{-1} = \underline{A}$

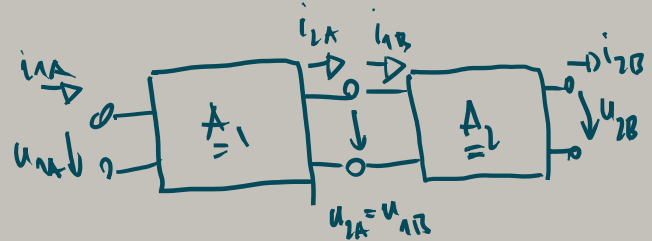

$$\begin{pmatrix} u_{1A} \\ i_{1A} \end{pmatrix} = \underline{A}_1 \cdot \begin{pmatrix} u_{2A} \\ i_{2A} \end{pmatrix} = \underline{A}_1 \cdot \left(\underline{A}_2 \cdot \begin{pmatrix} u_{2B} \\ i_{2B} \end{pmatrix} \right)$$

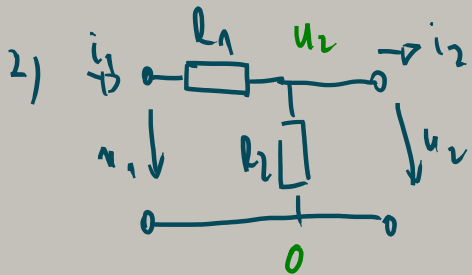
$\underline{A}_{12} = \underline{A}_1 \cdot \underline{A}_2$






$$\left. \begin{array}{l} ① \quad u_2 = u_1 - i_1 \cdot R_1 \\ ② \quad i_2 + \frac{1}{R_2} \cdot u_2 - i_1 = 0 \end{array} \right\} \underline{A} = \begin{pmatrix} 1 + \frac{R_1}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{pmatrix}$$

$$i_1 = \frac{1}{R_2} u_2 + i_2 \quad u_1 = u_2 + R_1 \left(\frac{1}{R_2} u_2 + i_2 \right) = \left(1 + \frac{R_1}{R_2} \right) u_2 + R_1 i_2$$

Feldbatterien:

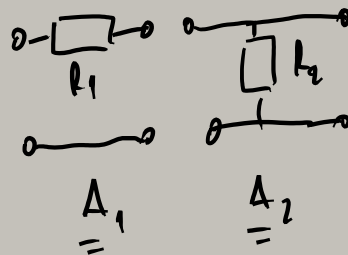

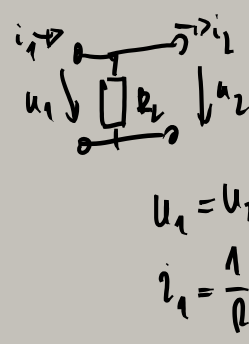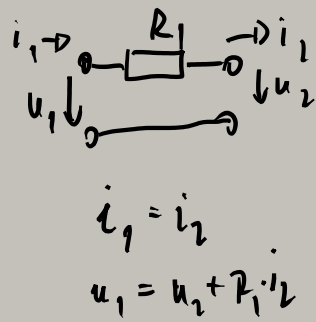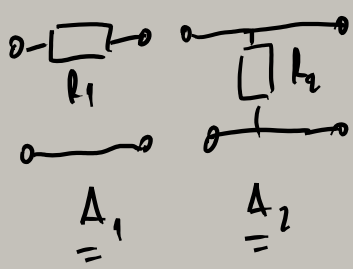

$$i_1 = i_2$$

$$u_1 = u_2 + R_1 \cdot i_2$$

$$A_1 = \begin{pmatrix} 1 & R_1 \\ 0 & 1 \end{pmatrix}$$

$$u_1 = u_2$$

$$i_1 = \frac{1}{R_2} u_1 + i_2$$

$$A_2 = \begin{pmatrix} 1 & 0 \\ \frac{1}{R_2} & 1 \end{pmatrix}$$

$$A_{\text{ges}} = \begin{pmatrix} 1 & R_1 \\ 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} 1 & 0 \\ \frac{1}{R_2} & 1 \end{pmatrix} = \begin{pmatrix} 1 \cdot 1 + R_1 \cdot \frac{1}{R_2} & 1 \cdot 0 + R_1 \cdot 1 \\ 0 \cdot 1 + 1 \cdot \frac{1}{R_2} & 0 \cdot 0 + 1 \cdot 1 \end{pmatrix} = \begin{pmatrix} 1 + \frac{R_1}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{pmatrix}$$

2.) $H \rightarrow A$




$$\left. \begin{aligned} u_1 &= H_{11} \cdot i_1 + H_{12} \cdot u_2 \\ i_2 &= H_{21} \cdot i_1 + H_{22} \cdot u_2 \end{aligned} \right\} \begin{aligned} H_{21} \cdot i_1 &= -H_{22} \cdot u_2 + i_2 \\ i_1 &= -\frac{H_{22}}{H_{21}} \cdot u_2 - \frac{1}{H_{21}} \cdot i_{2V} \end{aligned}$$

$$u_1 = H_{11} \left(-\frac{H_{22}}{H_{21}} \cdot u_2 - \frac{1}{H_{21}} \cdot i_{2V} \right) + H_{12} \cdot u_2$$

$$A = \begin{pmatrix} \frac{H_{21} \cdot H_{12} - H_{11} \cdot H_{22}}{H_{21}} & -\frac{H_{11}}{H_{21}} \\ -\frac{H_{22}}{H_{21}} & -\frac{1}{H_{21}} \end{pmatrix}$$

$$u_1 = \left(H_{12} - \frac{H_{11} \cdot H_{22}}{H_{21}} \right) u_2 - \frac{H_{11}}{H_{21}} \cdot i_{2V}$$

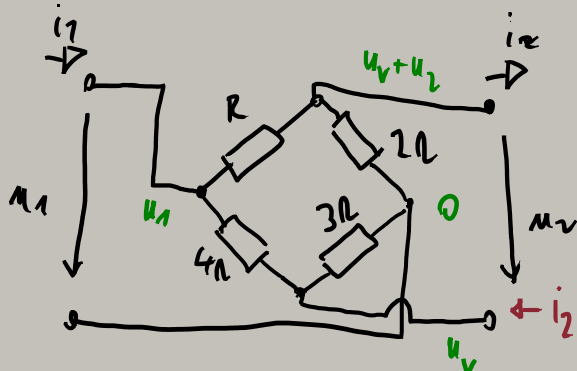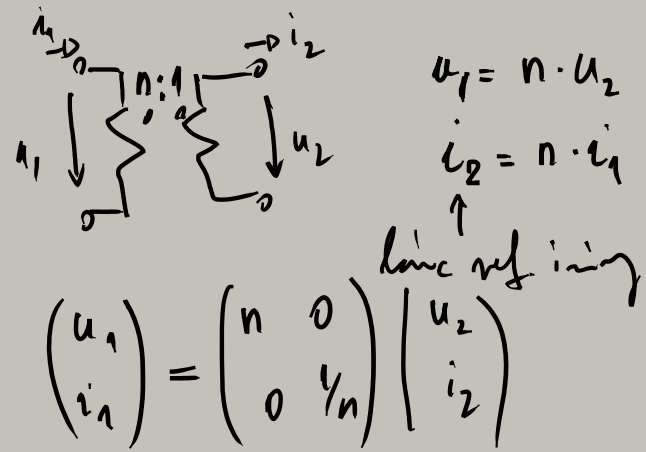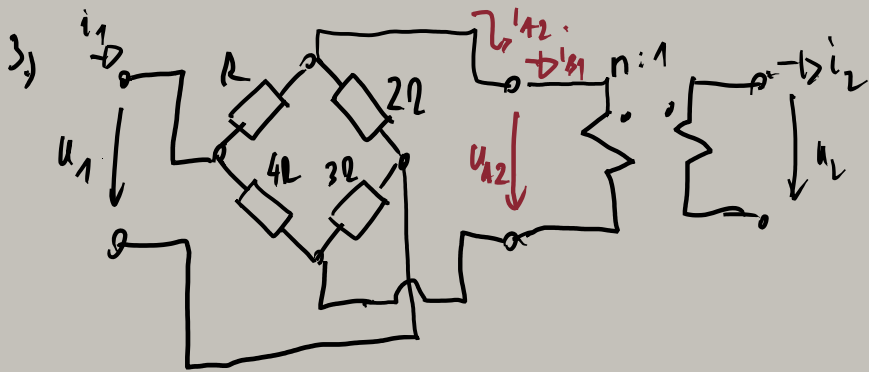$H_{21} \neq 0$, heißt A invertierbar! $\frac{1}{H_{21}}$



$$\textcircled{3} \rightarrow \textcircled{2} \quad -2u_1 + 3 \cdot \frac{3u_1 + 42R i_2}{7} + 3u_2 + 2R i_2 = 0$$

$$\underbrace{\left(2 - \frac{9}{7}\right)}_{5/7} u_1 = 3u_2 + R i_2 \left(2 + \frac{36}{7}\right) \rightarrow u_1 = \frac{3}{5/7} u_2 + \frac{50}{7} R \cdot i_2 \cdot \frac{7}{5}$$

$\underbrace{\hspace{1.5cm}}_{245} \qquad \underbrace{\hspace{1.5cm}}_{102 R i_2}$

$$\left. \begin{aligned} \textcircled{1} \quad -i_1 + \frac{u_1 - (u_V + u_2)}{R} + \frac{u_1 - u_V}{4R} &= 0 \\ \textcircled{2} \quad i_2 + \frac{(u_V + u_2) - u_1}{R} + \frac{u_V + u_2}{2R} &= 0 \\ \textcircled{3} \quad -i_2 + \frac{u_V - u_1}{4R} + \frac{u_V}{2R} &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} 5u_1 - 5u_V - 4u_2 - 42R i_1 &= 0 \\ -2u_1 + 3u_V + 3u_2 + 2R i_2 &= 0 \\ -3u_1 + 7u_V - 12R \cdot i_2 &= 0 \end{aligned} \right\}$$

$$\rightarrow \textcircled{1} \quad 42R i_1 = 5 \left(\frac{21}{5} u_2 + 102R i_2 \right) - 5 \cdot \frac{1}{7} \left(3 \cdot \left\{ \frac{21}{5} u_2 + 102R i_2 \right\} + 12R i_2 \right) - 4u_2$$


$$i_1 = \frac{1}{42R} (u_2) \left(21 - \frac{63}{7} - 4 \right) + i_2 \left(\frac{50 - \frac{5}{7} \cdot 42}{-4} \right)$$

$$u_V = \frac{3u_1 + 12R i_2}{7}$$

rendezés után:

$$A_{=1} = \begin{pmatrix} 4,2 & 10\Omega \\ 2/R & 5 \end{pmatrix}; \quad A_{=2} = \begin{pmatrix} n & 0 \\ 0 & 1/n \end{pmatrix}$$
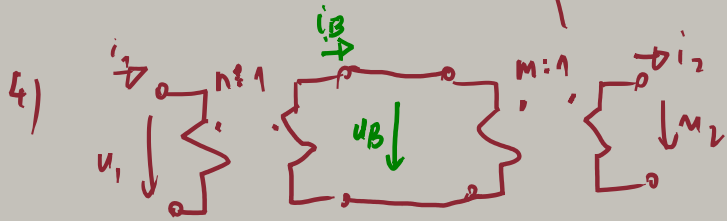
$$A_{=} = A_{=1} \cdot A_{=2} = \begin{pmatrix} n \cdot 4,2 & \frac{1}{n} \cdot 10\Omega \\ \frac{2}{R} \cdot n & 5/n \end{pmatrix} = \begin{pmatrix} 4,2 \cdot n & \frac{10\Omega}{n} \\ \frac{2n}{R} & 5/n \end{pmatrix}$$



$$\begin{pmatrix} n & 0 \\ 0 & 1/n \end{pmatrix} \cdot \begin{pmatrix} m & 0 \\ 0 & 1/m \end{pmatrix}$$

$$\begin{pmatrix} n \cdot m & 0 \\ 0 & \frac{1}{m \cdot n} \end{pmatrix}$$


$$\left. \begin{aligned} u_1 &= n \cdot u_B \\ i_B &= n \cdot i_1 \\ i_2 &= m \cdot i_B \\ u_B &= m \cdot u_2 \end{aligned} \right\}$$

$$u_1 = n \cdot m \cdot u_2$$

$$\frac{i_2}{m} = n \cdot i_1 \rightarrow i_1 = \frac{1}{m \cdot n} \cdot i_2$$

$$A_{=} = \begin{pmatrix} n \cdot m & 0 \\ 0 & \frac{1}{m \cdot n} \end{pmatrix}$$

4/6

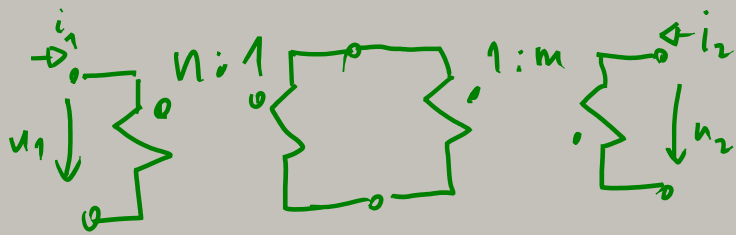

$$\begin{pmatrix} n & 0 \\ 0 & 1/n \end{pmatrix}$$


$$\begin{pmatrix} -1/m & 0 \\ 0 & -m \end{pmatrix}$$

$m:1$
↓
 $1:m$

$$\begin{pmatrix} -1/n & 0 \\ 0 & -1/m \end{pmatrix}$$


lässt
referenzierung

$m \rightarrow \frac{1}{m}$ nicht?

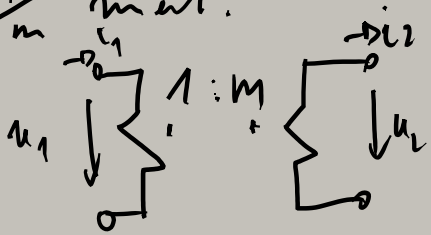

$$\left. \begin{aligned} u_2 &= m \cdot u_1 \\ i_1 &= m \cdot i_2 \end{aligned} \right\}$$
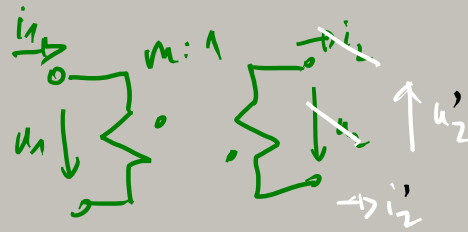
$$\begin{aligned} u_1 &= \frac{1}{m} \cdot u_2 \\ i_2 &= \frac{1}{m} \cdot i_1 \end{aligned}$$



$$\begin{aligned} i_2' &= -i_2 \\ u_2' &= -u_2 \end{aligned}$$

$$\begin{aligned} u_1 &= m \cdot u_2' = m \cdot (-u_2) = (-m) \cdot u_2 \\ i_2' &= m \cdot i_1 = m \cdot (-i_2) = (-m) \cdot i_2 \end{aligned}$$

$$\begin{pmatrix} n & 0 \\ 0 & 1/n \end{pmatrix} \quad \begin{pmatrix} -m & 0 \\ 0 & -1/m \end{pmatrix}$$

$$A = \begin{pmatrix} -n \cdot m & 0 \\ 0 & -\frac{1}{n \cdot m} \end{pmatrix}$$