

$$\underline{R} = \begin{pmatrix} 5 & 8 \\ -2 & 7 \end{pmatrix} \Omega$$

$$R_g = 5 \text{ k}\Omega$$

$$R_1 = 10 \text{ k}\Omega; U_0 = 20 \text{ V}$$

$$R_2 = 2 \text{ k}\Omega$$

egyenletrendszer:

"bal oldali  
"Kiering"  
"Kiering"

$$U_0 - R_g \cdot I_1 = U_1 \quad (1)$$

jobb oldali  
"Kiering"

$$U_2 = (-I_2) \cdot R_1 \times (R_1 + R_2) \quad (2)$$

$$20 - I_1 \cdot 5 = U_1$$

$$U_2 + I_2 \cdot 10 \times 12 = 0$$

konduktivitási

$$U_1 = R_{11} \cdot I_1 + R_{12} \cdot I_2 \quad (3) \rightarrow U_1 = 5 I_1 + 8 I_2$$

$$U_2 = R_{21} \cdot I_1 + R_{22} \cdot I_2 \quad (4) \rightarrow U_2 = -2 I_1 + 7 I_2$$

Egyenletrendszer

$$10 \times 12 = \frac{120}{12} = \frac{60}{11}$$


$$U_0 - R_g \cdot I_1 = U_1$$

$$U_2 = (-I_2) \cdot (R_1 \times (R_1 + R_2)) \quad (1)$$

$$U_1 = R_{11} \cdot I_1 + R_{12} \cdot I_2$$

$$U_2 = R_{21} \cdot I_1 + R_{22} \cdot I_2$$

$$\begin{pmatrix} 1 & 5 & \cdot & \cdot \\ \cdot & \cdot & 1 & 60/11 \\ -1 & 5 & \cdot & 8 \\ \cdot & 2 & 1 & -7 \end{pmatrix} \cdot \begin{pmatrix} U_1 \\ I_1 \\ U_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 20 \\ \cdot \\ \cdot \\ \cdot \end{pmatrix} \Rightarrow \begin{pmatrix} U_1 \\ I_1 \\ U_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 11,138 \text{ V} \\ 1,773 \text{ mA} \\ -1,5524 \text{ V} \\ 0,2846 \text{ mA} \end{pmatrix}$$

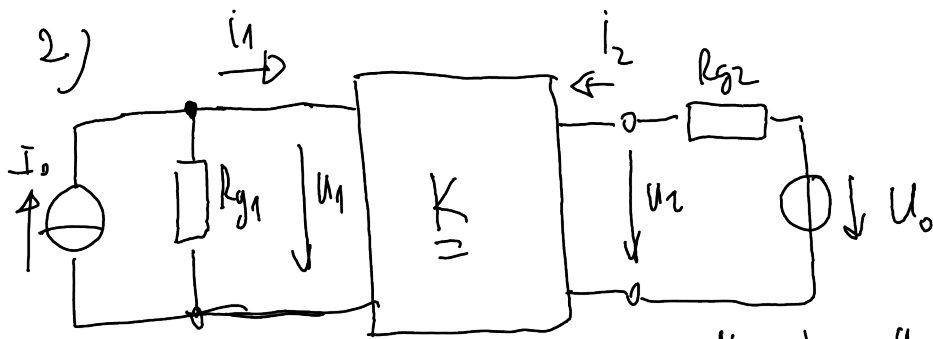

$$1) -I_0 + \frac{1}{R_{g1}} \cdot U_1 + I_1 = 0$$

$$2) U_2 - U_0 = -I_2 \cdot R_{g2}$$

$$3) I_1 = K_{11} \cdot U_1 + K_{12} \cdot I_2$$

$$4) U_2 = K_{21} \cdot U_1 + K_{22} \cdot I_2$$

$$\begin{pmatrix} \frac{1}{R_{g1}} & 1 & 0 & 0 \\ 0 & 0 & 1 & R_{g2} \\ K_{11} & -1 & 0 & K_{12} \\ K_{21} & 0 & -1 & K_{22} \end{pmatrix} \begin{pmatrix} U_1 \\ I_1 \\ U_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} I_0 \\ U_0 \\ 0 \\ 0 \end{pmatrix}$$

Egyenletek


$$-I_0 + \frac{1}{R_{g1}} \cdot U_1 + I_1 = 0 \quad (1)$$

$$U_2 - U_0 = -I_2 \cdot R_{g2} \quad (2)$$

$$I_1 = K_{11} \cdot U_1 + K_{12} \cdot I_2 \quad (3)$$

$$U_2 = K_{21} \cdot U_1 + K_{22} \cdot I_2 \quad (4)$$
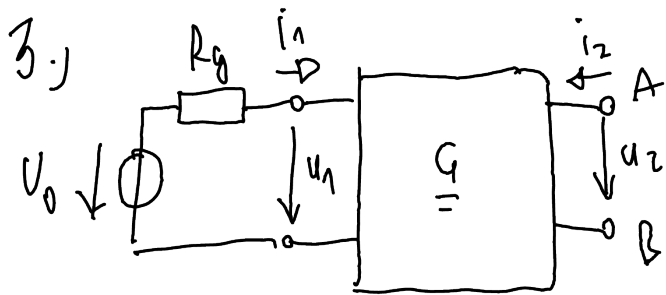
$$\begin{pmatrix} 0,1 & 1 & \cdot & \cdot \\ \cdot & \cdot & 1 & 5 \\ 0,2 & -1 & \cdot & -0,5 \\ 1 & \cdot & -1 & 1 \end{pmatrix} \cdot \begin{pmatrix} U_1 \\ I_1 \\ U_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 5 \\ 100 \\ \cdot \\ \cdot \end{pmatrix} \Rightarrow \begin{pmatrix} U_1 \\ I_1 \\ U_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 34,7826V \\ 1,5217mA \\ 45,6522V \\ 10,8696mA \end{pmatrix}$$



$$U_0 = 10V$$

$$R_g = 2k\Omega$$

$$G = \begin{pmatrix} 5 & 4 \\ 7 & 8 \end{pmatrix} mS$$

• Thévenin - h.t.

• Norton - h.t

-  $2k\Omega, 1V, mA$  egyszerű

$$\textcircled{1} U_0 - I_1 \cdot R_g - U_1 = 0$$

$$\textcircled{2} I_2 = 0$$

$$\textcircled{3} I_1 = G_{11} \cdot U_1 + G_{12} \cdot U_2$$

$$\textcircled{4} I_2 = G_{21} \cdot U_1 + G_{22} \cdot U_2$$

$$\textcircled{2}^* U_2 = 0$$

$$I_{r2} = -I_2$$

$$I_N = -I_{r2} = I_2$$

$$U_T = U_2$$

szakadás

Szakadással történő lezárás ( $I_2 = 0$ )

$$U_0 - I_1 \cdot R_g - U_1 = 0 \quad (1)$$


$$I_2 = 0 \quad (2)$$

$$I_1 = G_{11} \cdot U_1 + G_{12} \cdot U_2 \quad (3)$$

$$I_2 = G_{21} \cdot U_1 + G_{22} \cdot U_2 \quad (4)$$

Üresjárási feszültség :

$$U_T = U_2 = -2.1875V$$

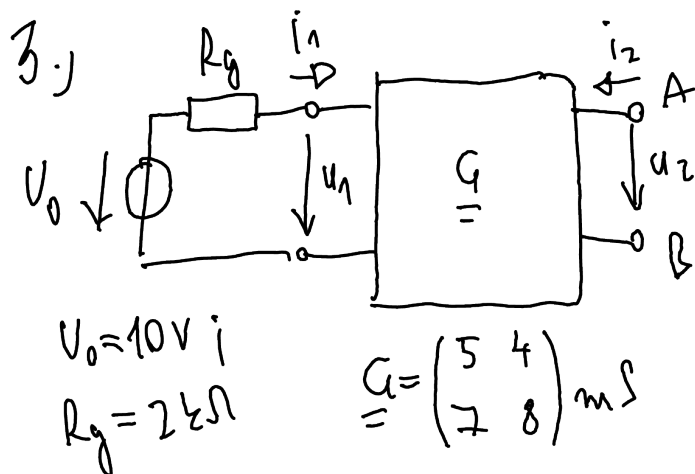

• Thévenin - h.t.  
 • Norton - h.t.  
 -  $k\Omega, V, mA$  egység

$\rightarrow U_T = U_2$

Rövidzárral történő lezárás ( $I_2 = 0$ )

$$U_0 - I_1 \cdot R_g - U_1 = 0 \quad (1)$$

$$I_2 = 0 \quad (2)$$

$$I_1 = G_{11} \cdot U_1 + G_{12} \cdot U_2 \quad (3)$$

$$I_2 = G_{21} \cdot U_1 + G_{22} \cdot U_2 \quad (4)$$

Rövidzát árama :

$$I_N = -I_{rz} = -(-I_2) = I_2 = 6.3636mA$$

$R_B$  számítása :

$$R_B = -\frac{U_T}{I_N} = -\frac{-2,1875V}{6,3636mA} = 0,3438k\Omega$$

